
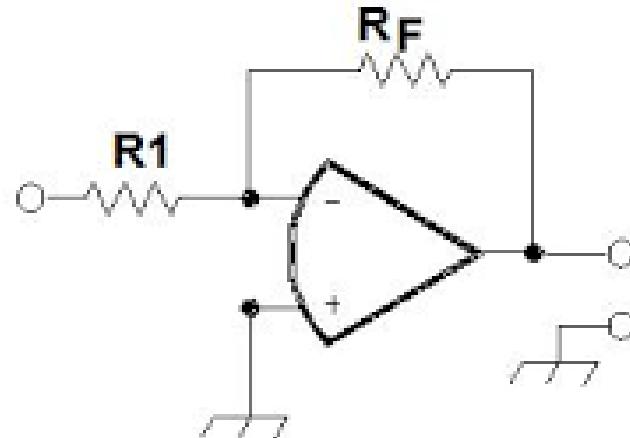

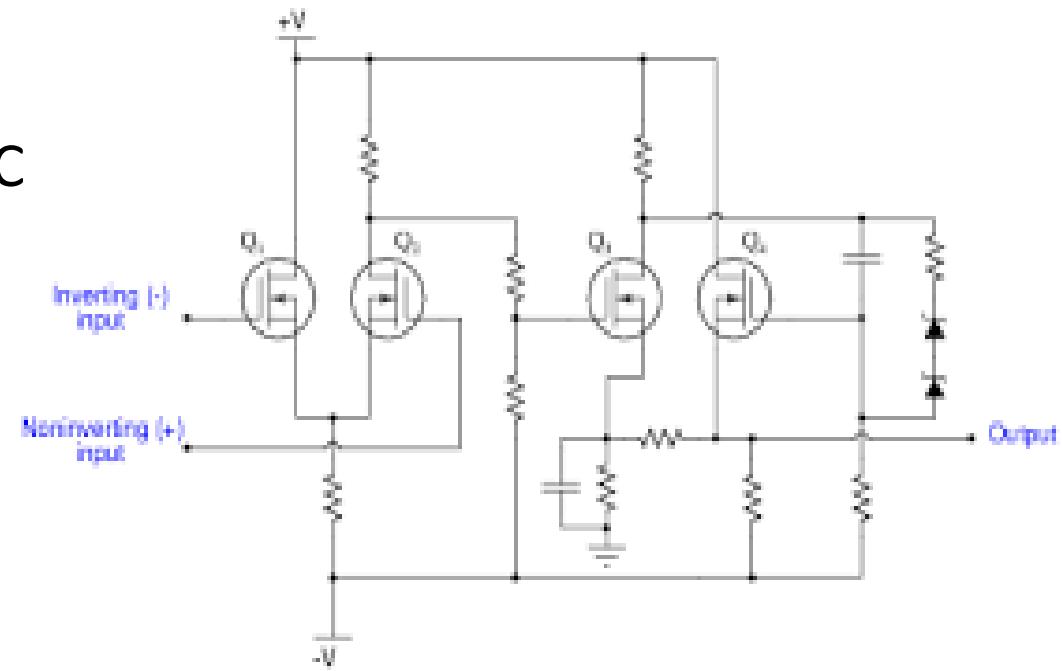
# The Operational Amplifier When, Why, What, Who ?




Emil Novakov  
UGA / IMEP-LAHC



# Milestones

- Feed Back Electronic circuits – H. Black, 1928, Bell Labs, Philips
- « Long-tailed-pair » - differential amplifier, J. Toennies, 1938
- First Op Amp, Loebb Julie, 1941 (gun director - military applications)
- Birth of the term “Operational Amplifier”, J. Ragazzini, 1947
- OP Amp Model K2-W, G. A. Philbrick, GAP/R, 1952
- Model 130, the world's first transistorized op-amp, Burr Brown, 1958
- P45, transistorized Op Amp, Bob Peace, GAP/R, 1961
- First monolithic Op Amp  $\mu$ A 702, B. Widlar, Fairchild, 1963, ( $\mu$ A 709 – 1965)
- World standard  $\mu$ A741, D. Fulagar, Fairchild, 1968
- Model 45, high speed JFET Op Amp, J. Cadigan, Analog Devices, 1970
- CA3130, the first CMOS Op Amp, O. Schade, RCA, 1974


# The feedback problem

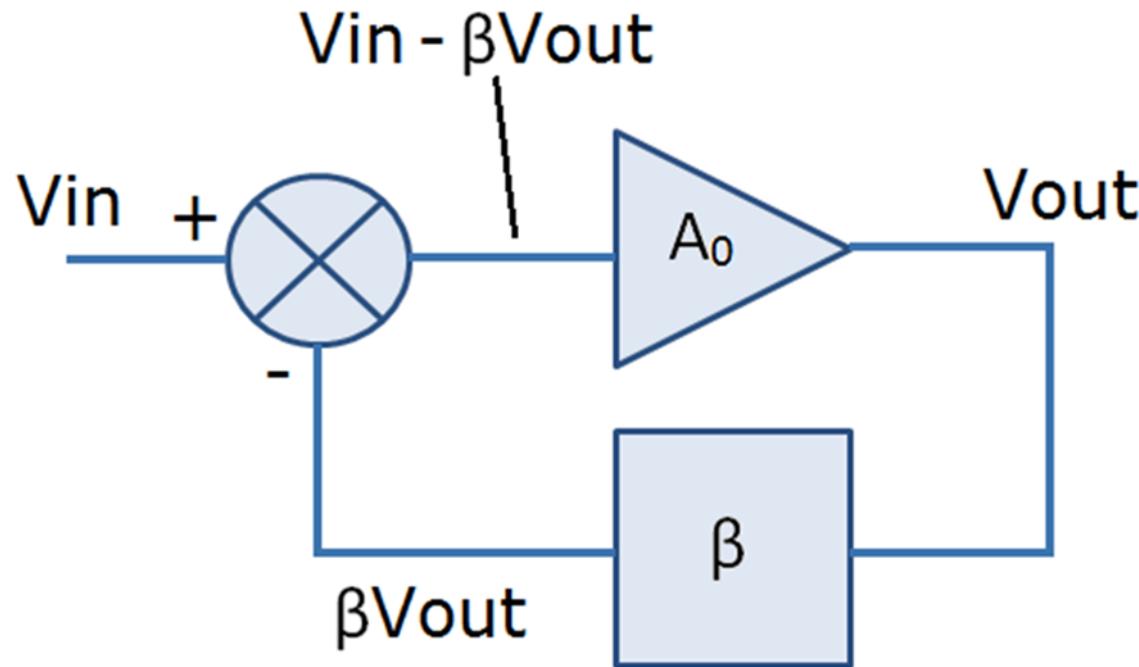

Paul Voigt : mid-1920s  
Alan Blumlein (GB) - 1930s  
A research group at Philips (Netherlands)  
H. Black - late 20s to early 30s.  
B. D. H. Tellegen 1937

Karl Dale Swartzel filed a patent for the 'summing amplifier', 1941, Bell Labs

# The basic electronic circuit

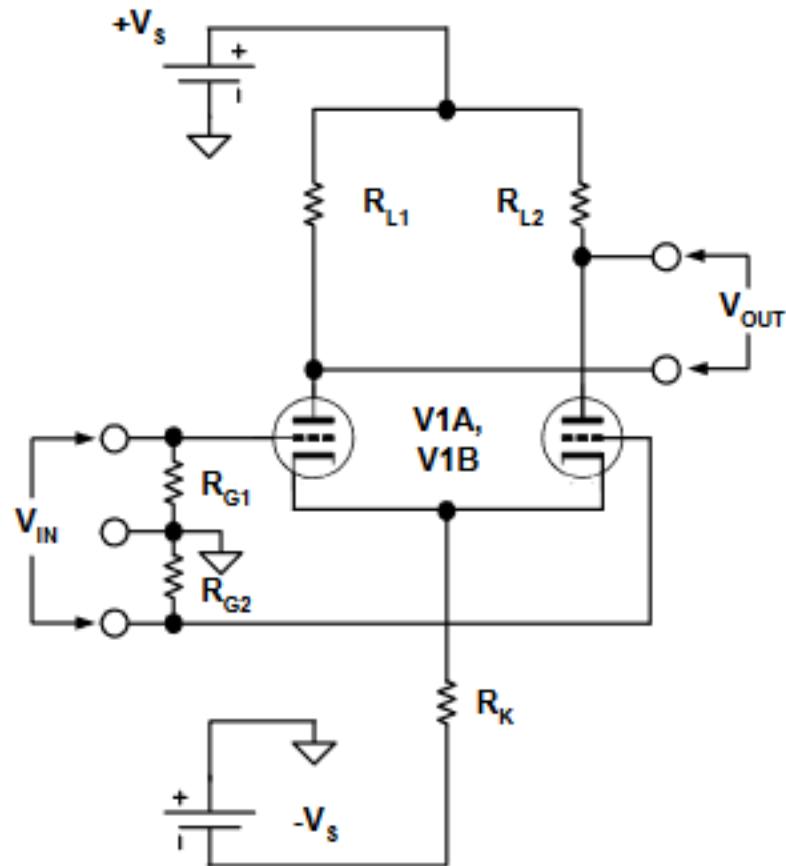


Cathode-coupled long-tailed differential pair  
1938 J. F. Toennies


Bell Labs 1941, Division 7 - M9 project  
Under George A. Philbrick supervision, Julie Loeb completed a two-tube op amp design, using a pair of dual triodes in a full differential-in / differential-out arrangement. The first operational amplifier.

# Two inputs amplifier

Symbol

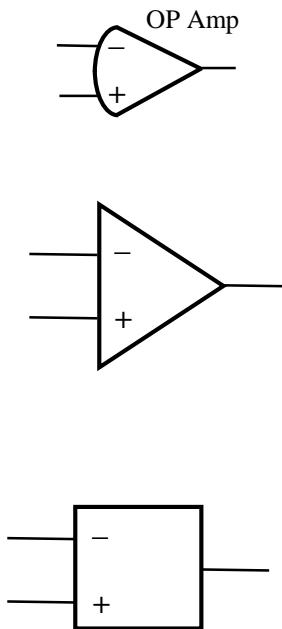


Model

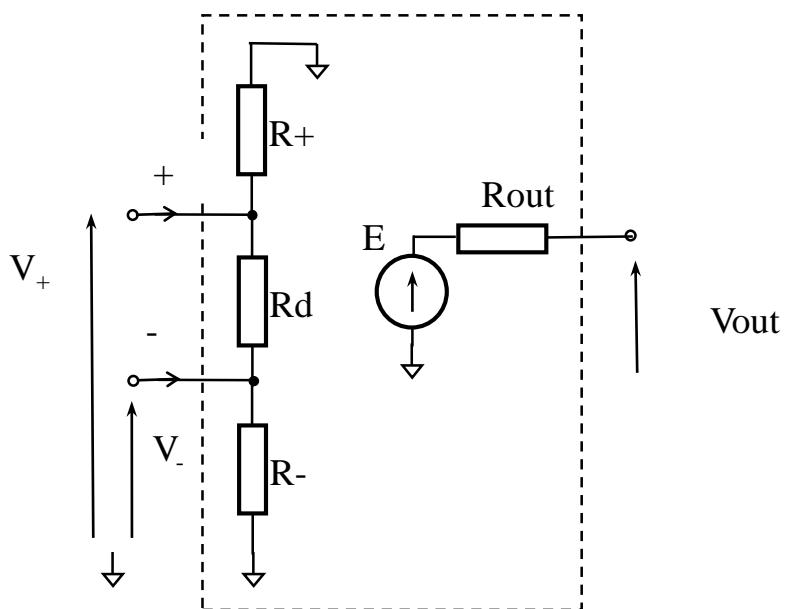

$$E = G_d(V_+ - V_-) + G_{cm}\left(\frac{V_+ + V_-}{2}\right)$$







Ideal Model

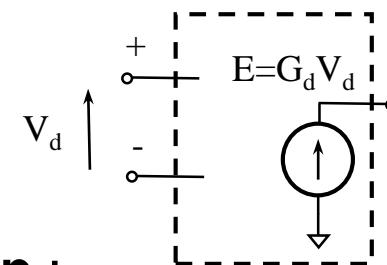


**Ideal Op Amp :**

- Voltage controlled voltage source with :
- infinite differential gain ( $G_d$ ) ,
- zero common mode gain ( $G_{cm}$ ),
- infinite input impedances ( $R_+$ ,  $R_-$ ,  $R_d$ ),
- zero output impedance ( $R_{out}$ ),
- infinite bandwidth
- zero offset ( $V_+ - V_- = 0 \rightarrow E = 0$ )

# Basic circuits - arithmetic operations

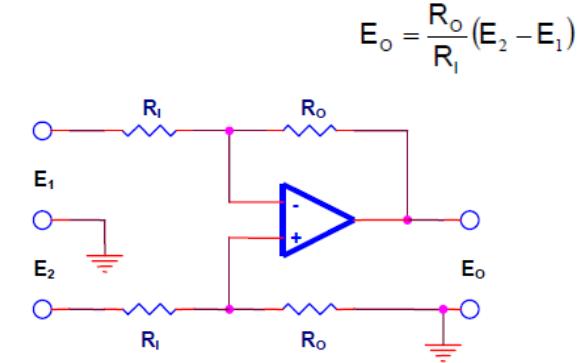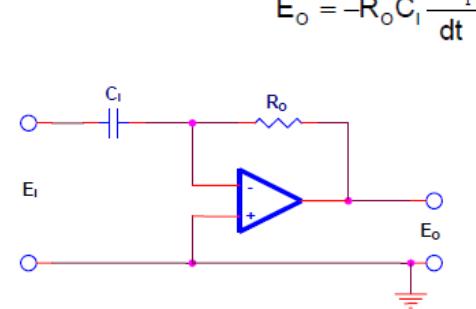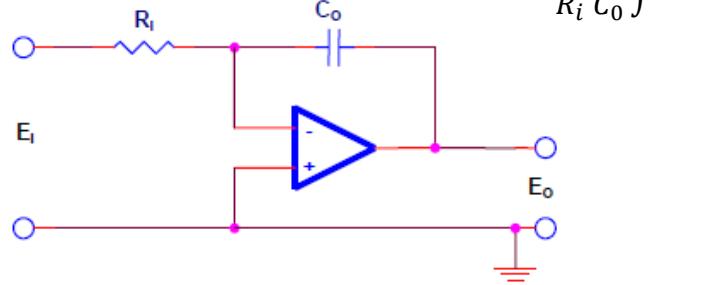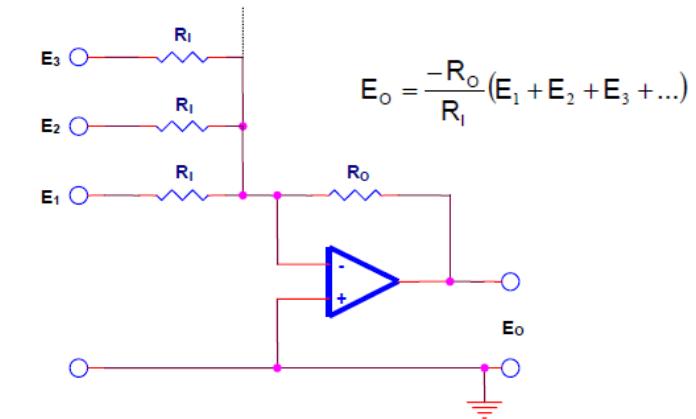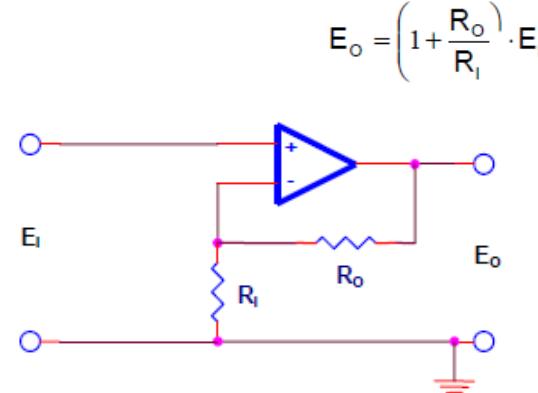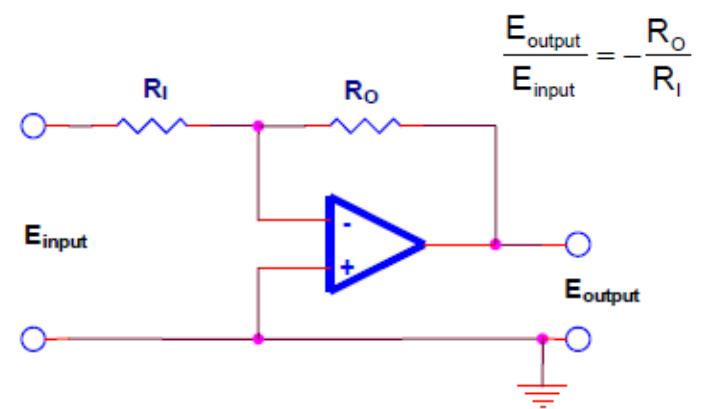


# Differential equation resolution

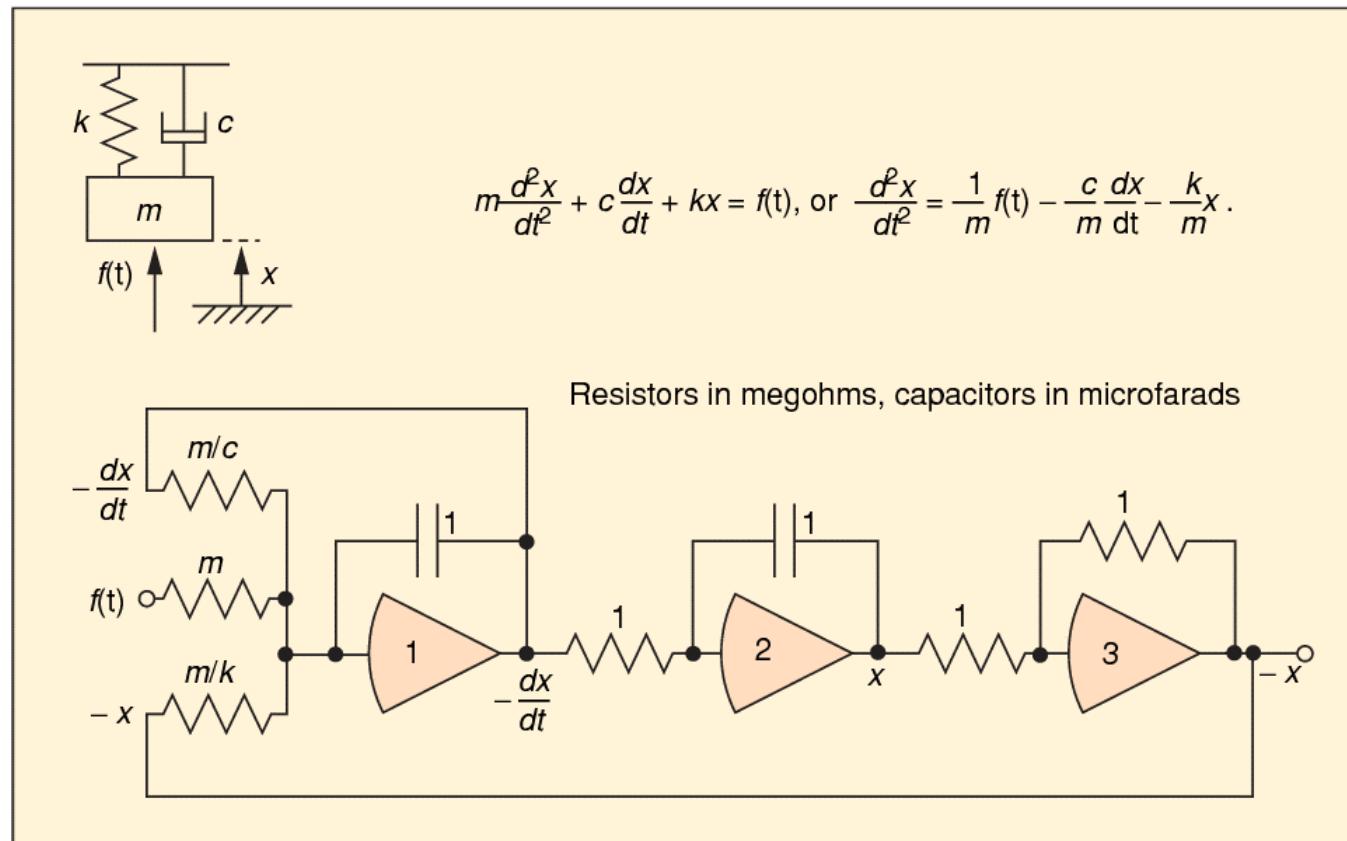

John Ragazzini (1947)  
Columbia University of New York

"As an amplifier so connected can perform the mathematical operations of arithmetic and calculus on the voltages applied to its input, it is hereafter termed an **'operational amplifier'**."

# The analog computer – V2 rocket

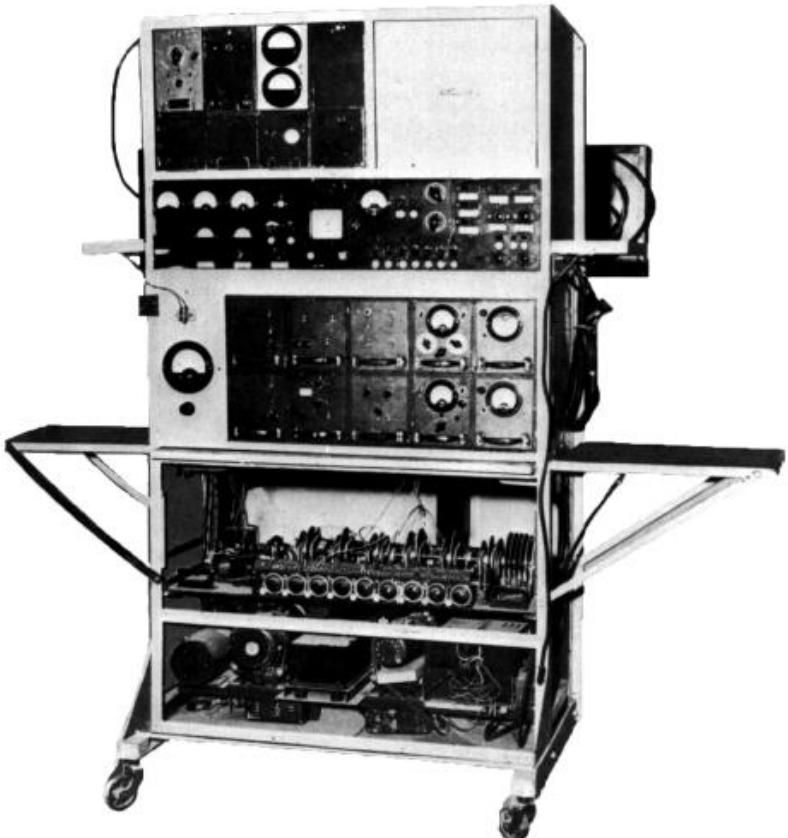

1941, Hoelzer analog computer (Peenemunde, Germany ):  
- V2 rocket dynamics simulation,  
- Calculate and simulate V2 trajectories.

The computer was based on an electronic integrator and differentiator conceived by Hoelzer in 1935.





Mischgeraet : the world's first  
on-board computer,  
guidance section of V2 rocket.

# The analog computer – M9 Gun Director



M9 Gun Director - D. Parkinson, Bell Labs, 1943.  
A revolutionary instrument !  
M9's radar tracked incoming enemy aircraft,  
determined their speed, altitude and direction  
and then relayed the information to an  
analog computer that calculated the anti-aircraft  
gun's trajectory and fuse setting. During one week  
in August 1944, M9s destroyed 89 of 91 V1 !
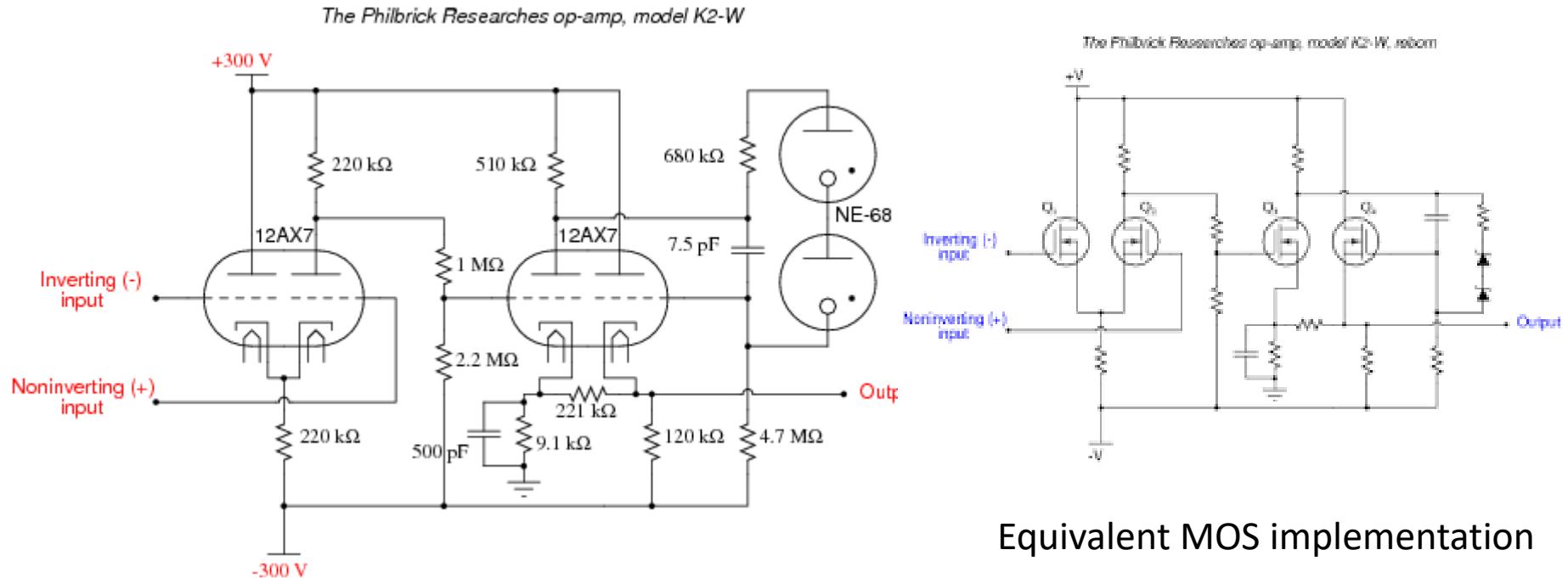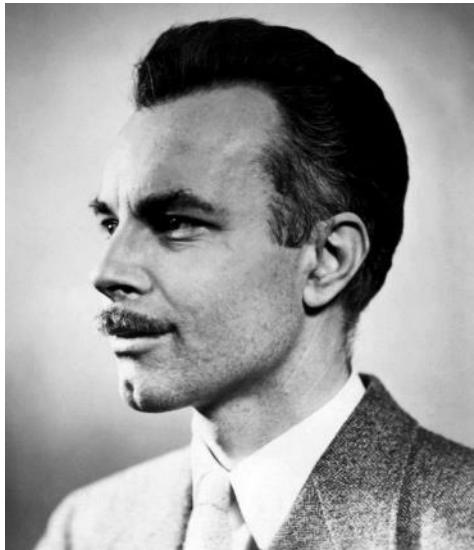
# G. A. Philbrick Research (GAP/R): K2-W Op Amp



Equivalent MOS implementation

1946, G. A. Philbrick started GAP/R - Analog Computers Company  
K2-W, 1952 commercial use of the Operational Amplifier, Price US\$ 20  
K2-W was last manufactured in 1971


# The analog computer




PACE 16-31R, 1950s  
Electronic analog computer,  
Electronic Associates Inc.,  
NASA's Lewis Flight Propulsion Laboratory,  
Used in Mercury, Gemini, and  
Apollo programs.
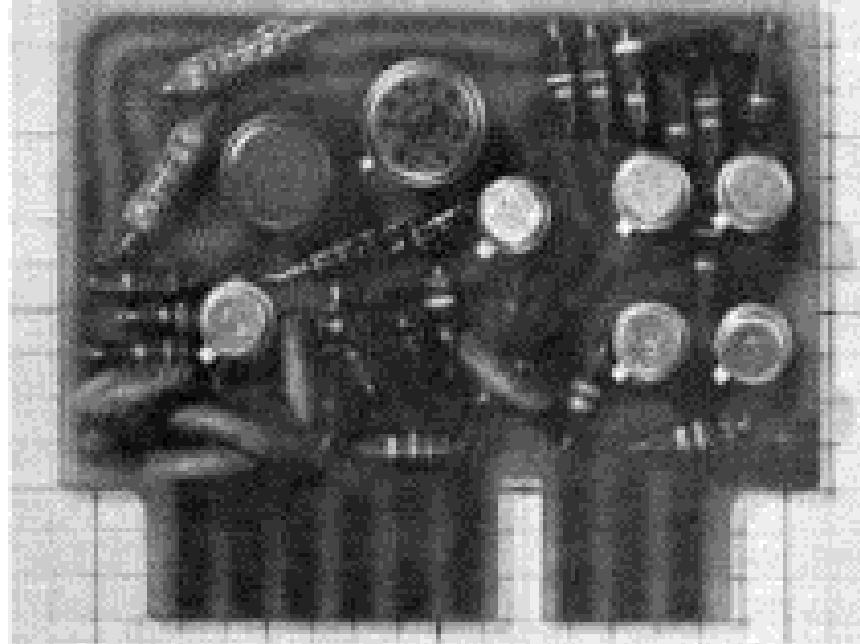
# Solid state modular and hybrid amplifiers

- 1947, J. Bardeen, W. Brattain, W. Shockley, Bell Labs - The transistor
- 1954, G. Teal, Texas Instruments : grown - junction silicon transistor




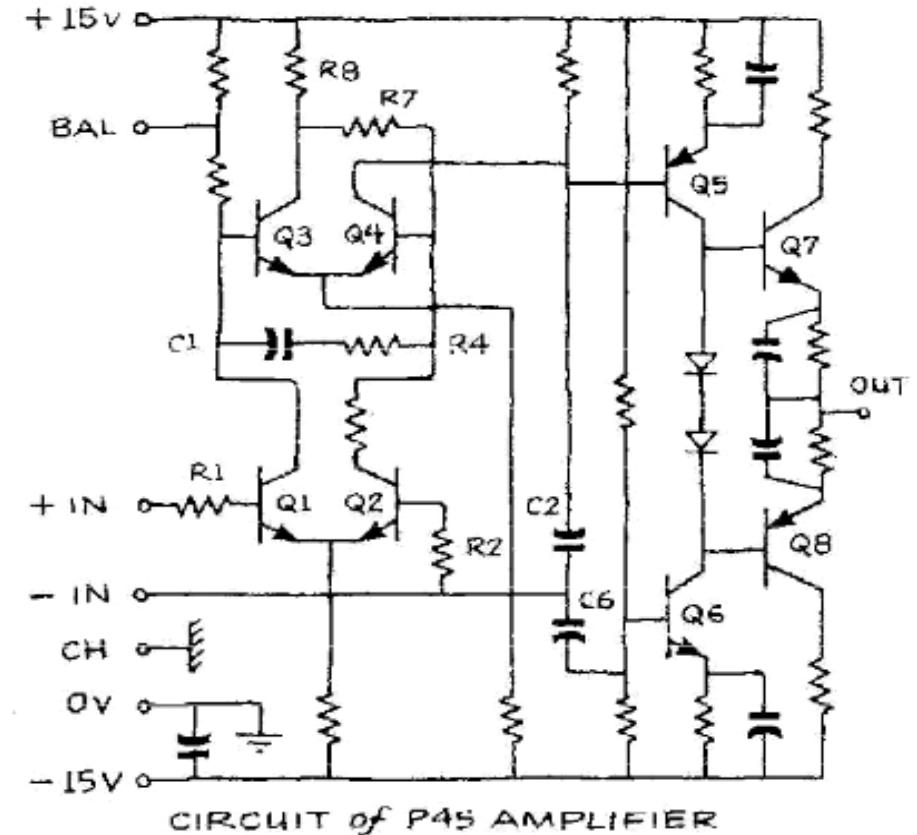1961, P45, Bob Pease, GAP/R First transistorized op amp



CIRCUIT OF P45 AMPLIFIER
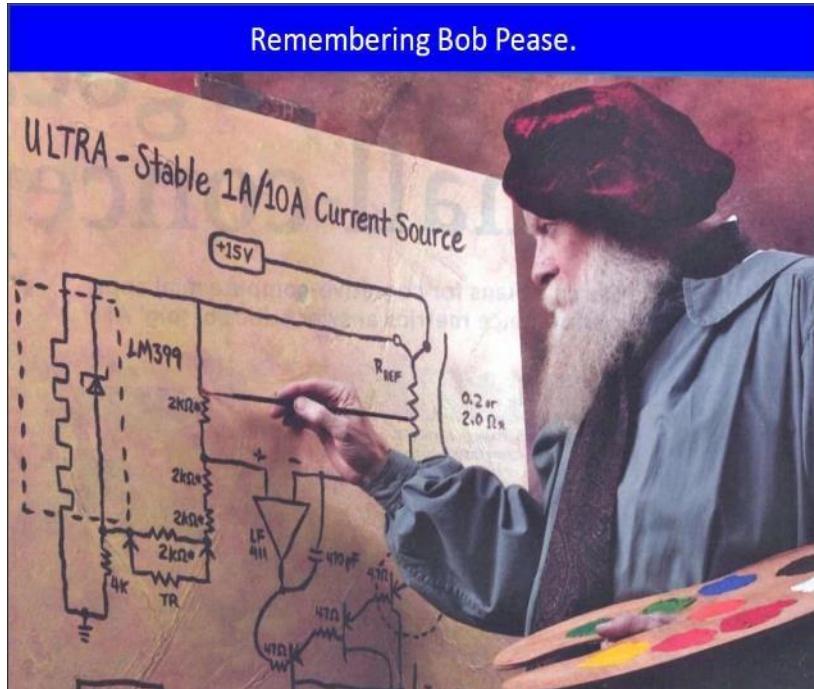
# Bob Pease - GAP/R, National Semiconductor




What's All This .... Stuff, Anyhow?

P45A could deliver  $\pm 10$  V at  $\pm 20$  mA to the load.  
Gain was rated a minimum of 50,000 at into a load of  $500 \Omega$ .  
Gain-bandwidth product of 100 MHz!  
In 1966, P45A cost \$118.  
P45 ran on  $\pm 15$  V, the new power standard.  
Input / output signals ranges of  $\pm 10$  V.


Bob Peace : Analog guru at National Semiconductor !  
Band-gap Reference Circuit Tsar  
LM337 regulator designer  
LM331 V-F converter and many other circuits ...  
Famous columnist at Electronic Design.

# NASA Op Amp's

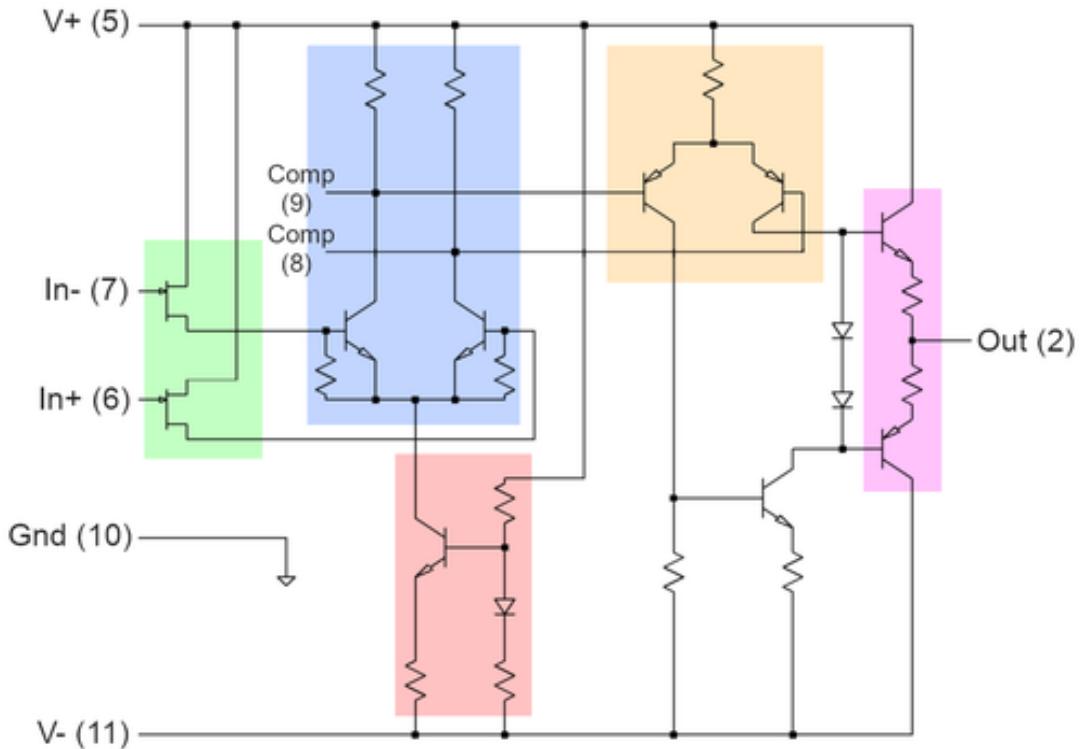

- 2404BG, 1969, Amelco, designed by Bob Peace 58,50 \$ (today 300 \$).
- 1966, Amelco + GAP/R → Teledyne Philbrick Nexus
- Apollo 12 on the Moon

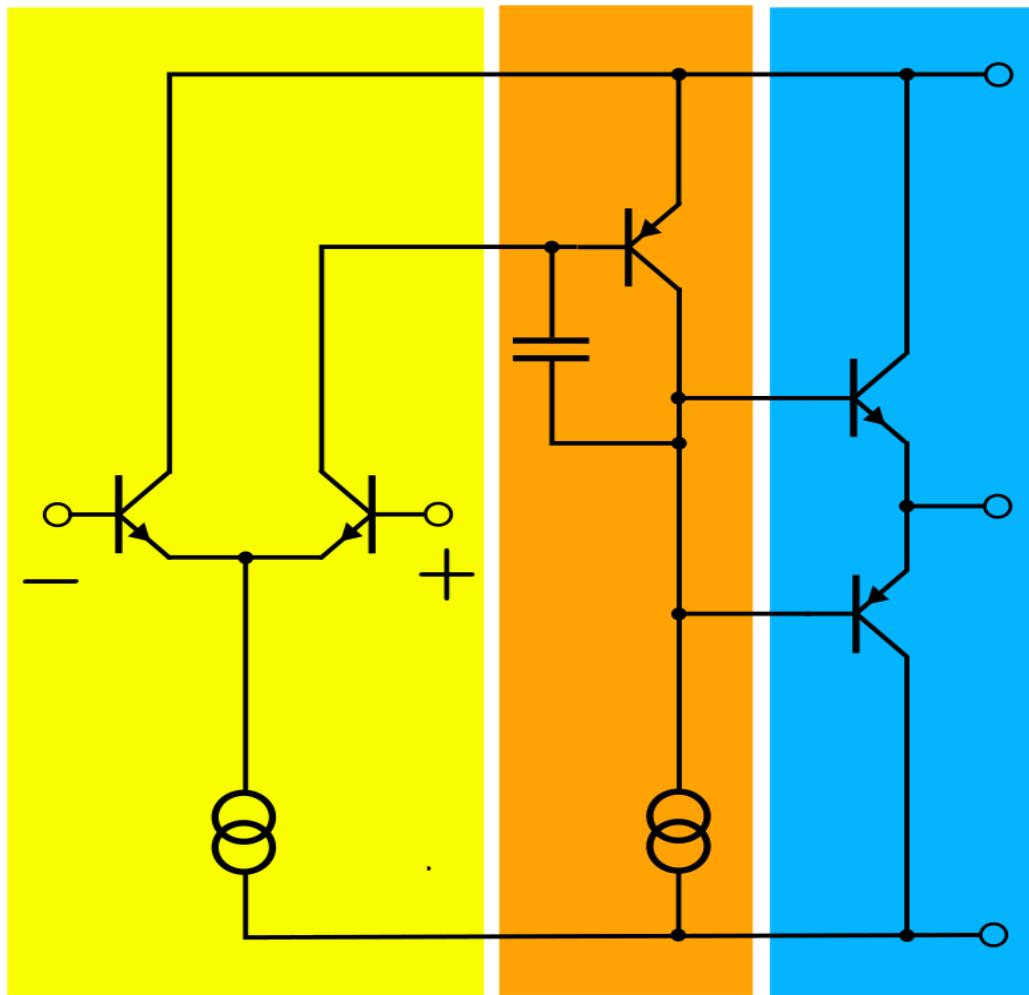
# Transistorized OP Amp – Basic structure



3 stages:

1. Differential input & gain
2. Gain and offset shift
3. Output stage

# The monolithic Op Amp

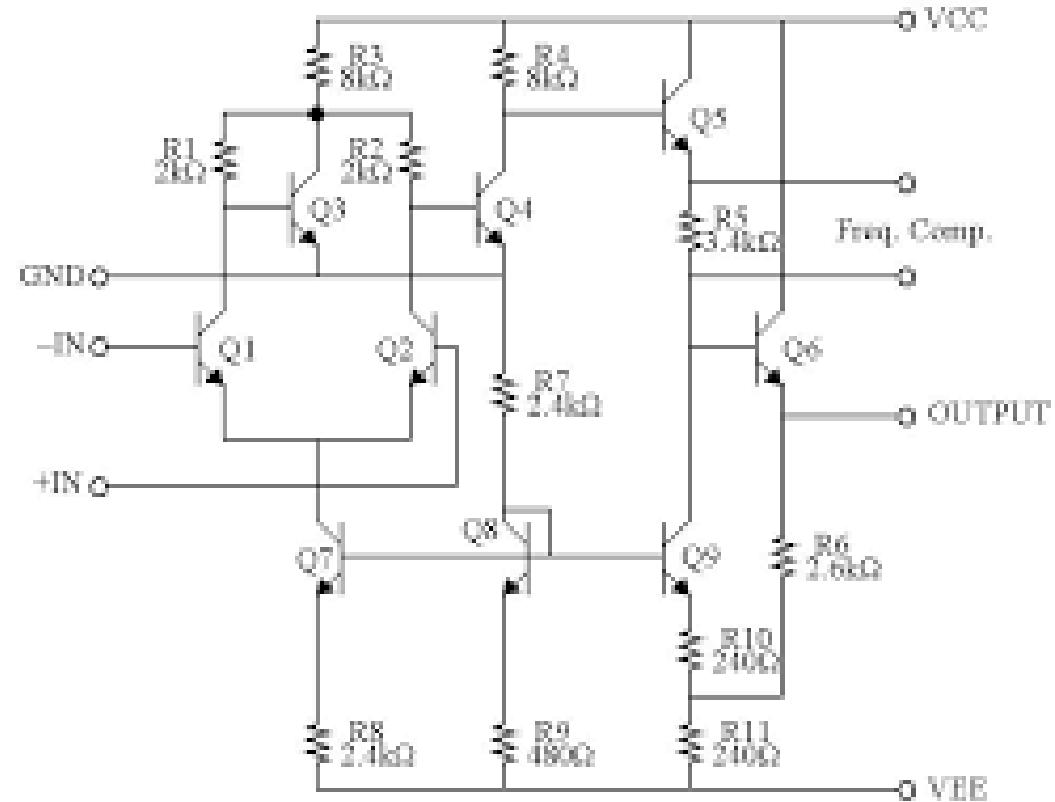


First monolithic Op Amp : μA702, Bob Widlar, 1963, 300 US\$ !

# Bob Widlar – the analog IC genius. “Digital? Every Idiot Can Count to One”



- 1963, Bob Widlar, Fairchild Semiconductor,
- First monolithic op Amp:  $\mu$ A702
- 1965,  $\mu$ A709, first commercial success.
- LM10, National Semiconductor, brilliant Op Amp designs, in production for over three decades
- Design of countless analog IC!


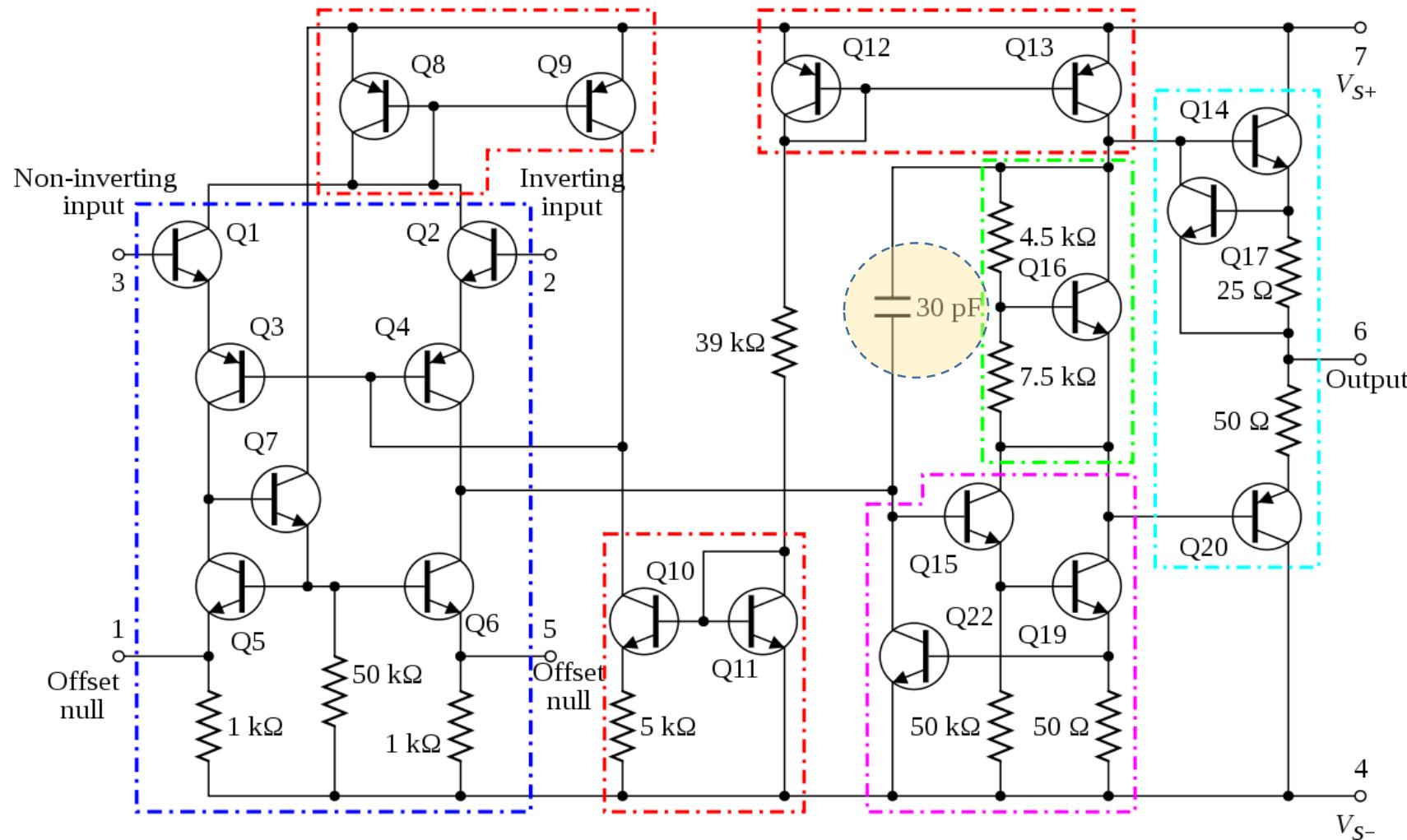
# $\mu$ A 741 – The legend (D. Fulagar, Fairchild, 1968)



Internal frequency  
compensation

Short circuit output protection

# $\mu$ A 741 - Layout

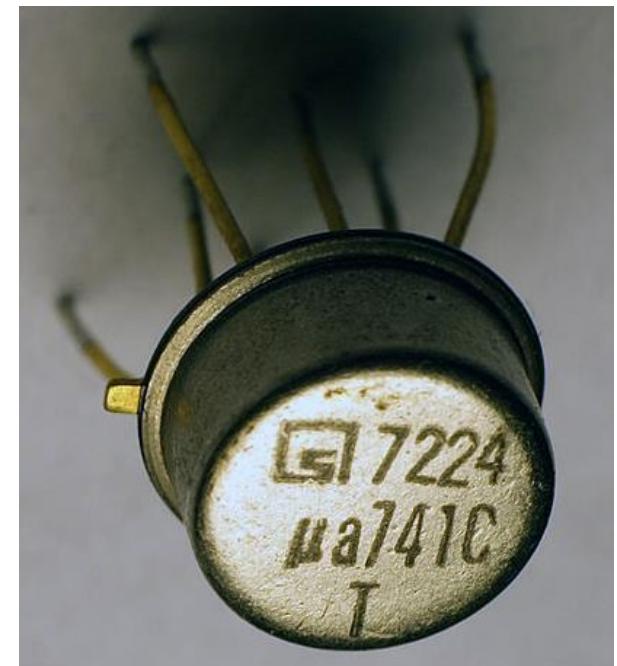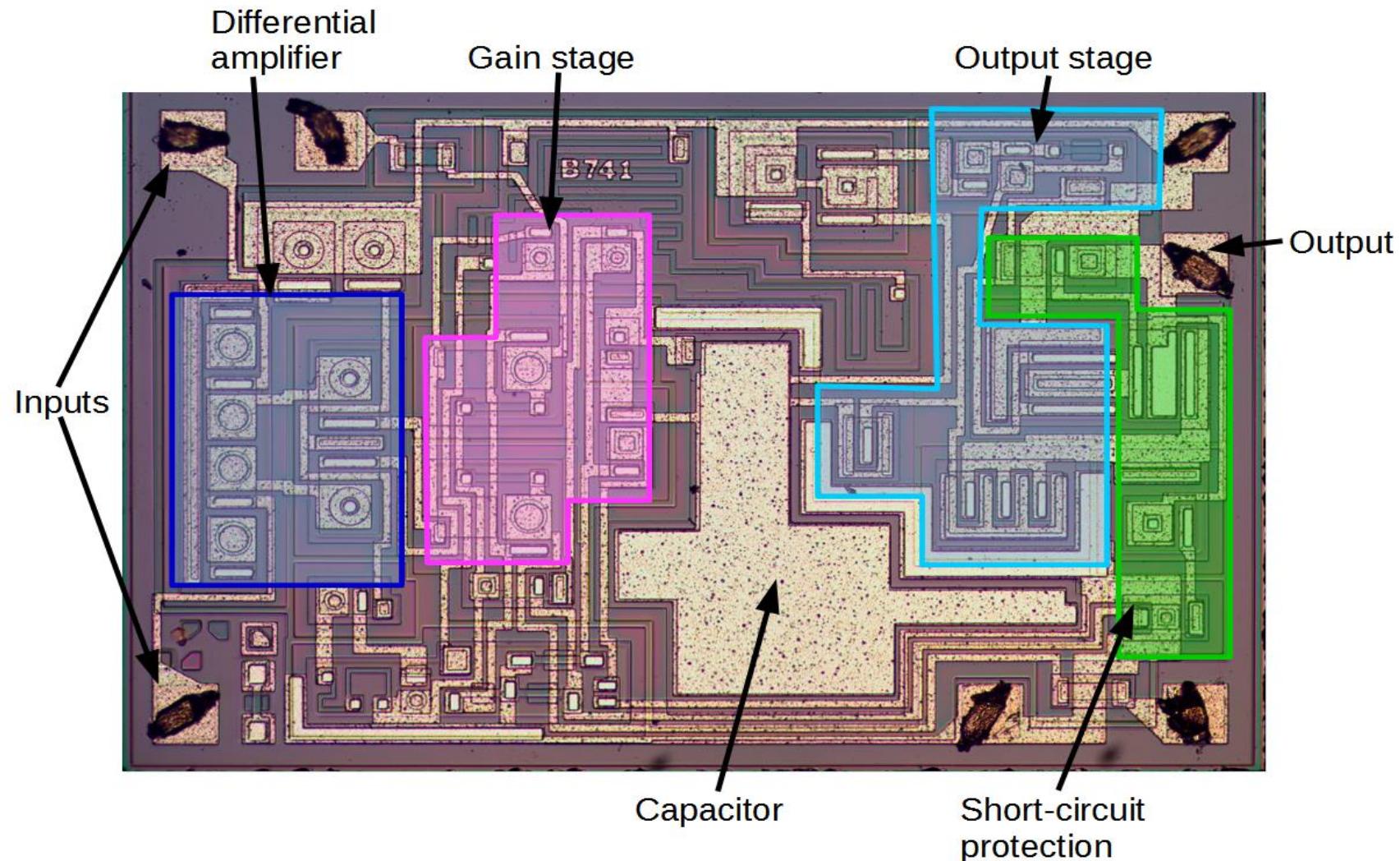

# $\mu$ A 741 today (2020) – still alive, 52 years later!


The screenshot shows the Farnell website interface. At the top left is the Farnell logo with the tagline "AN AVNET COMPANY". To the right is a search bar with dropdown menus for "Tous" (All), language (Chinese), and part number "741". Below the search bar is a navigation bar with links: "Tous les produits" (All products), "Fabricants" (Manufacturers), "Ressources" (Resources), and "Communauté" (Community). A breadcrumb navigation path is visible below the navigation bar: Accueil > Semiconducteurs - Circuits intégrés > Amplificateurs et Comparateurs > Amplificateurs opérationnels (AOP) > UA741CDT. The main content area displays the product name "UA741CDT - Amplificateur opérationnel, 1 amplificateur, 1 MHz, 0.5 V/μs, 5V à 40V, SOIC, 8 Broche(s)". To the left is a black SOIC-8 package image. To the right is a detailed product card for STMicroelectronics, showing fields for Manufacturer reference, Order code, Technical sheet, and a link to "Découvrez tous les docum".

2020, Price (per 1000) :  
0.12 EUR

$\mu$ A 741 Estimated sales:  
≈ US\$ 10 billion

≈ 20 billion circuits

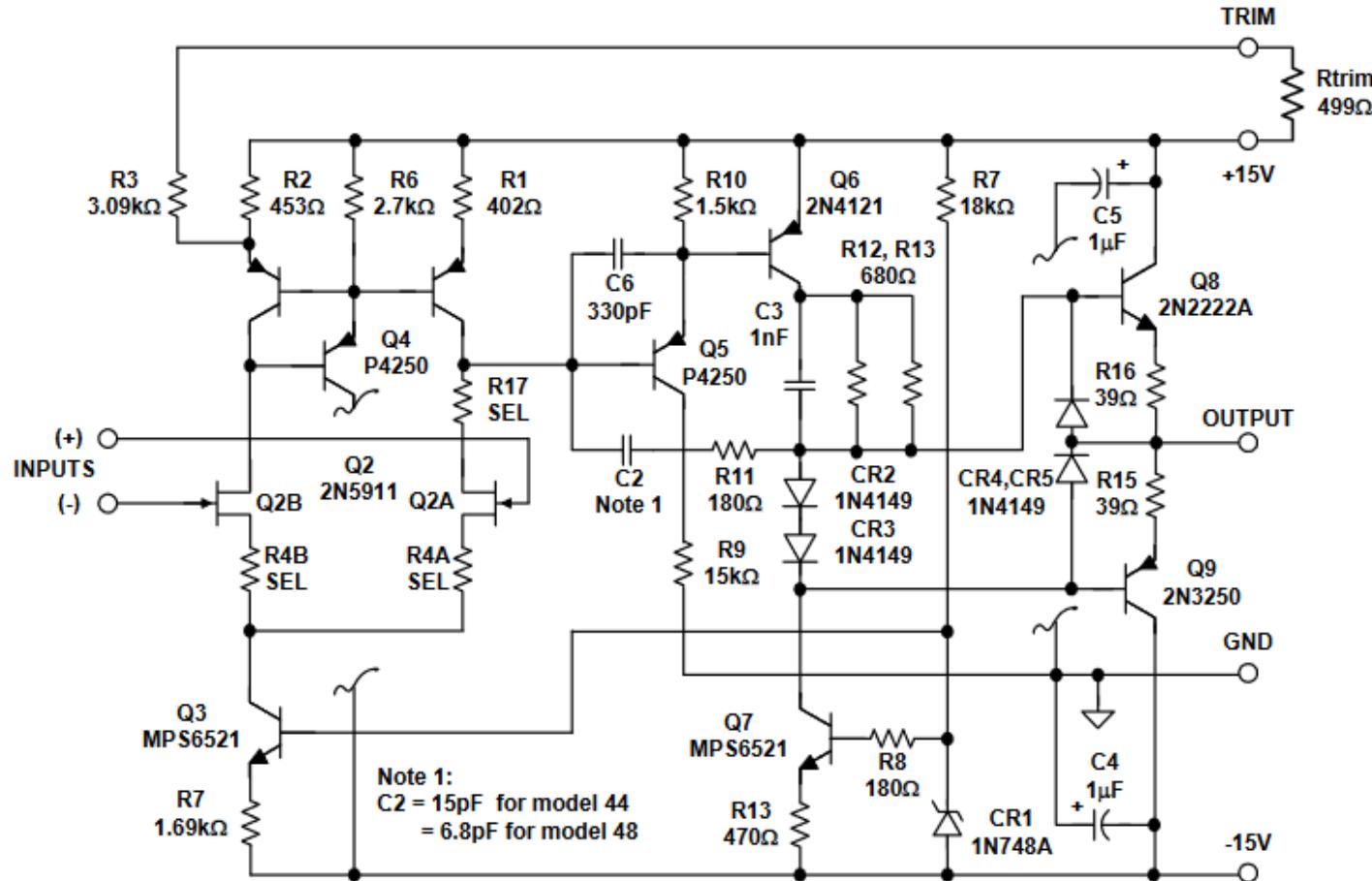
# Model 44 high speed JFET 110 V/ $\mu$ s



J. Cadigan,  
Analog Devices, 1970  
Very-low input currents

# CA3130 first CMOS Op Amp (pMOS input)

**Schematic Diagram**

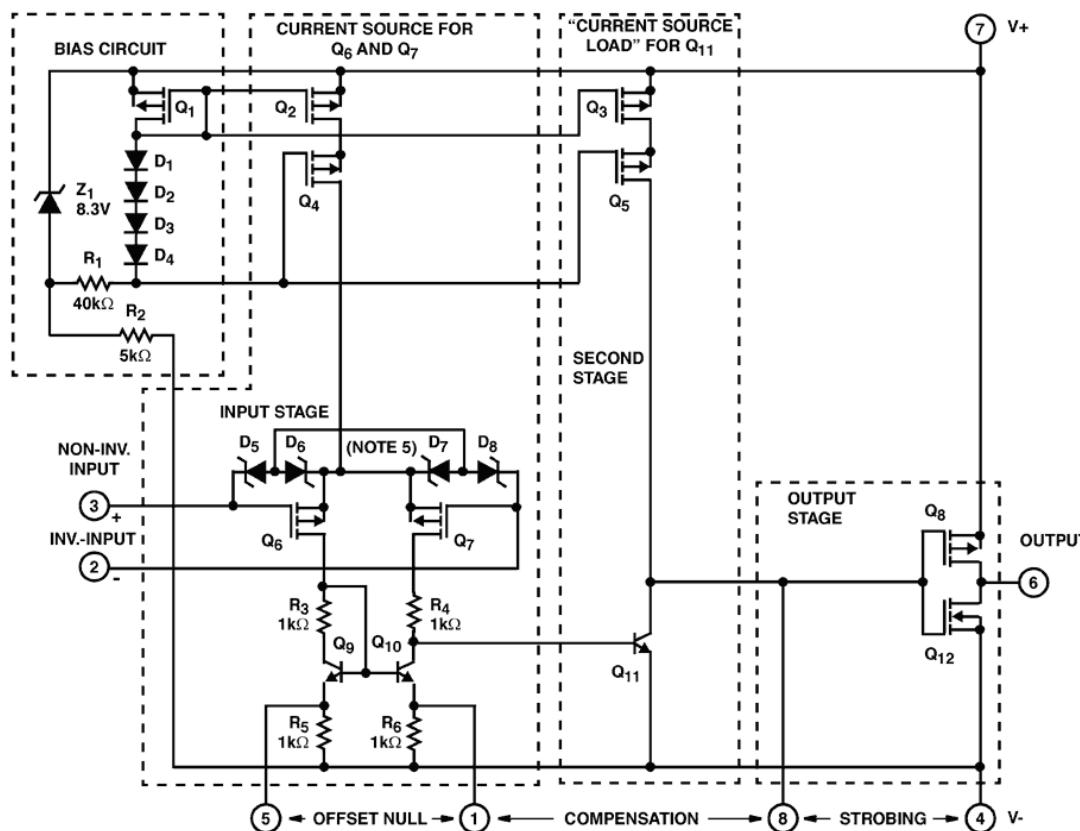


O. Schade, RCA, 1974

- Very High  $Z_{\text{Input}}$ ,  $1.5 \text{ T}\Omega$  ( $1.5 \times 10^{12}\Omega$ ) !
- Very Low  $I_{\text{Input}}$ , 2pA at 5V Operation


CMOS OP Amps are most frequently used as sub-circuits within larger systems : on-chip applications (ADC, DAC, Audio, voice ...)

Air-wiring to avoid leaks !

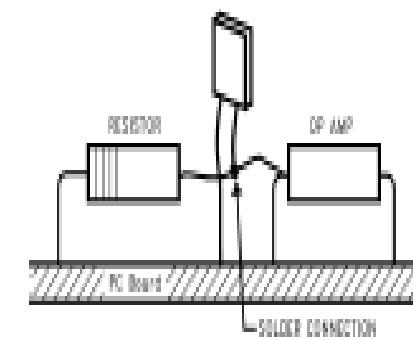
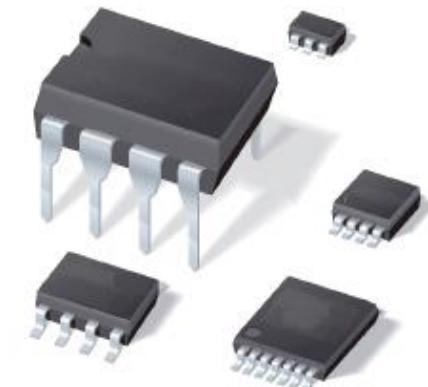
# Companies : merger & acquisition (and dead ...)

- GAP/R - George A. Philbrick Research, Philbrick - Nexus (+Amelco), Teledyne Philbrick, Teledyne semiconductor (E2V), Microchip.
- Fairchild (acquired by National Semiconductor)
- National Semiconductor (NS), acquired by Texas Instruments (TI) , 2011
- Analog Devices 5AD) (Ray Sata, 1965)
- Burr Brown (BB), acquired by Texas Instruments, 2000
- Maxim
- Linear Technology (LT), acquired by Analog Devices, 2016




2020: Main players: AD (+LT), Maxim, TI (+NS), Microchip, STMicroelectronics

# Op Amp: a good business !

- STMicroelectronics, 2019, “Analog, MEMS and Sensor group (AMS)”, US\$ 3.3 billion revenue (30%!), ST – US\$ 9.5 billions revenue.


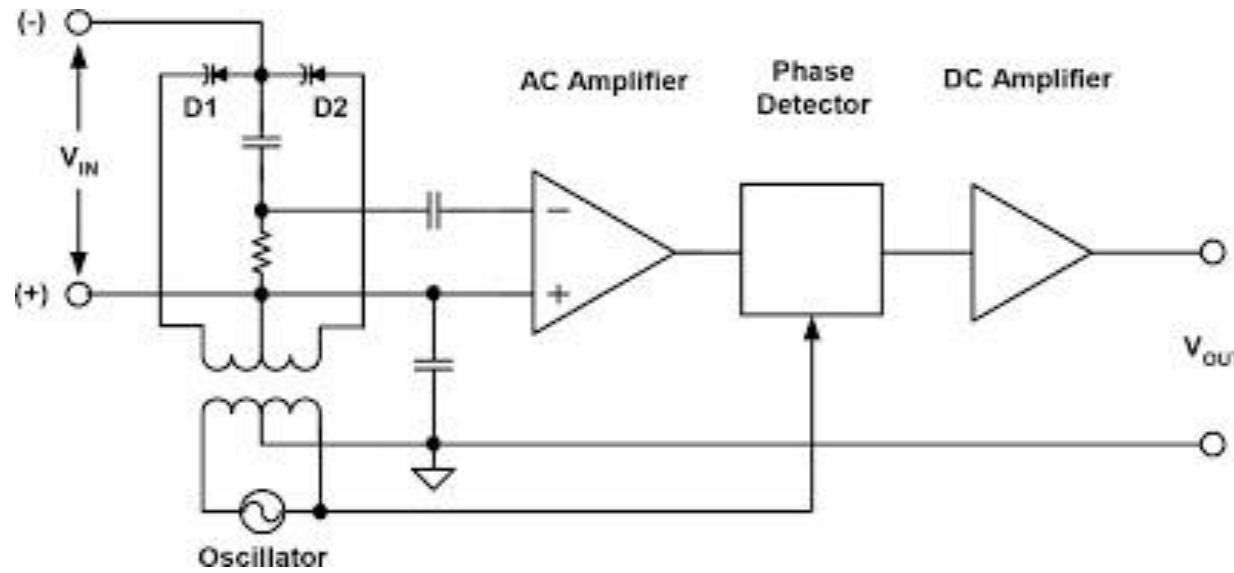
# Case Study 1: Varactor bridge amplifier P2




An idea of G. Philbrick

P2 Pico-ampere Input Current (Transducers signal processing)

Bob Malter, GAP/R , 1960 5-10 pA input, gain 10000, US\$ 227 dollars (average price of a car US\$ 2500)

P2 dominated for 30 years, becoming obsolete only after the release of the LMC660,  $I_{input} = 2 \text{ fA}$  – 1998!



# P2 schematics from Bob Peace

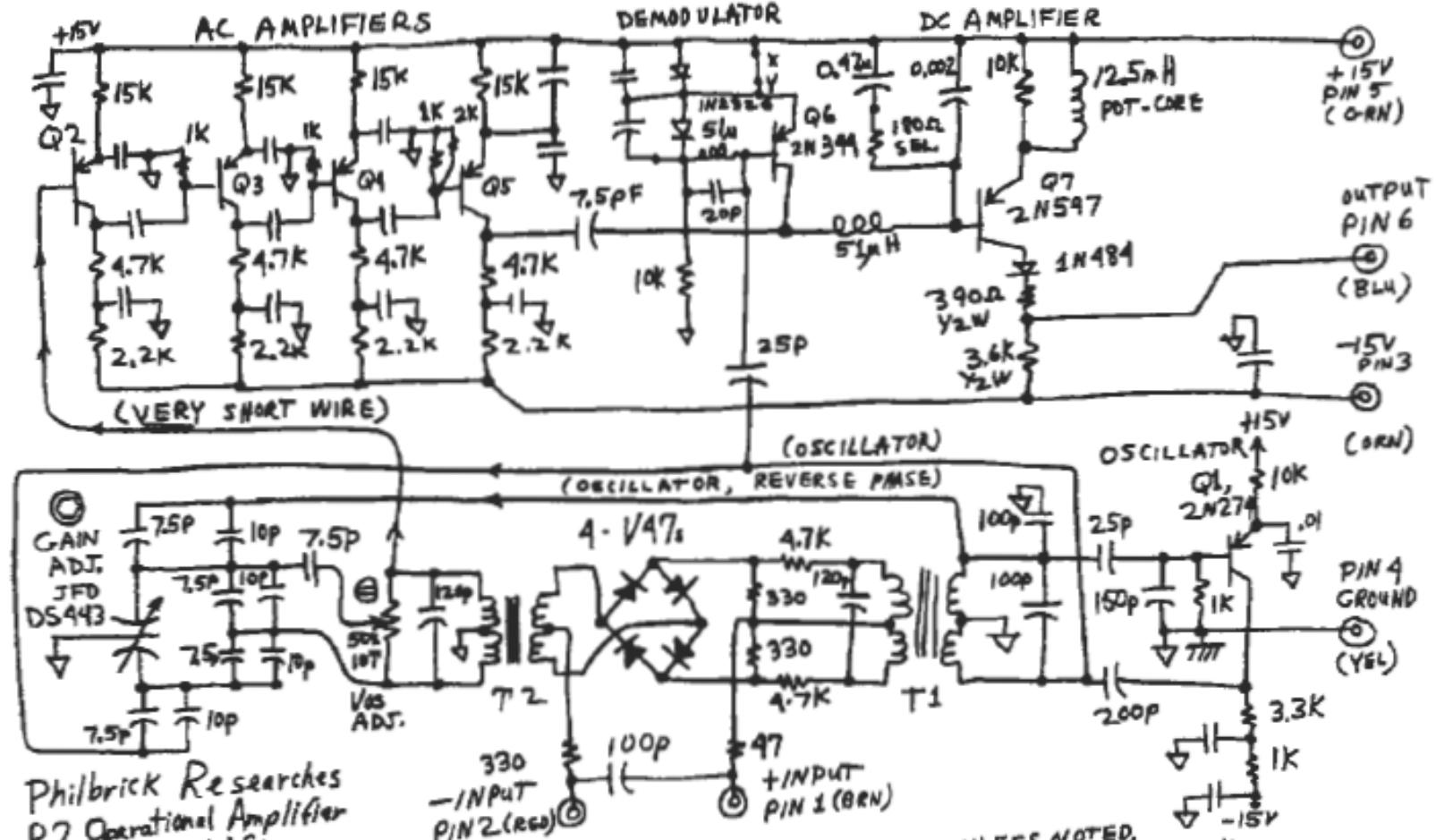




UNLESS NOTED,  
ALL RESISTORS  $\pm 5\%$ ,  $Y_{AW}$   
ALL CAPACITORS  $0.01\mu F$ , 50V  
ALL CERAMIC DISC  
ALL CAPACITORS SMALLER THAN  $160\mu F$   
ARE NOD CERAMIC OR SILVER MICA
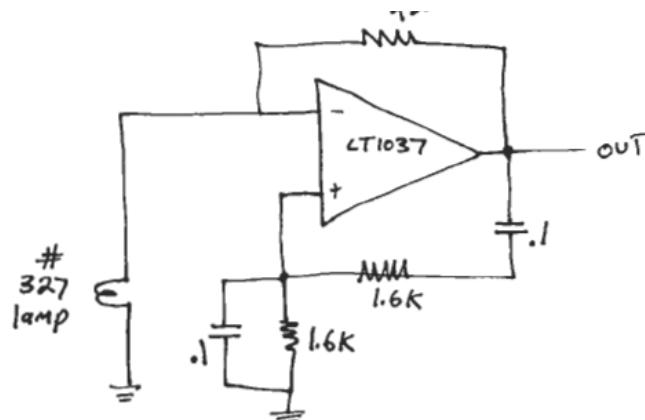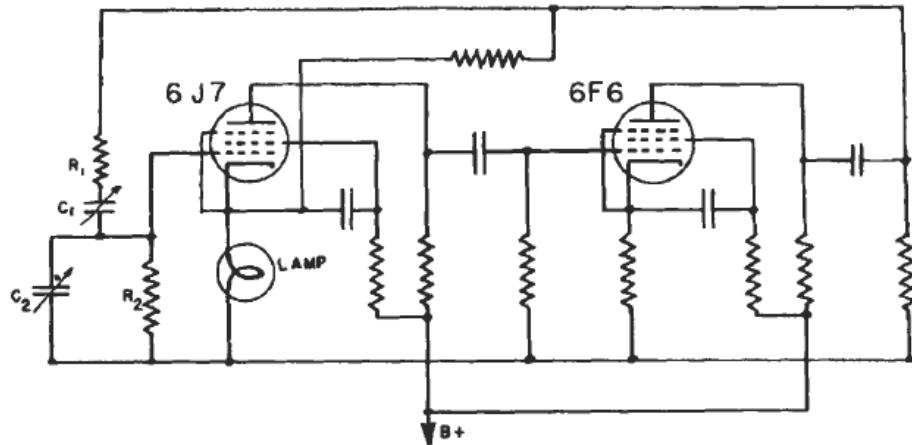
# Case study 2 :


Wien Bridge Oscillator, Bill Hewlett, Ph.D. thesis, 1939



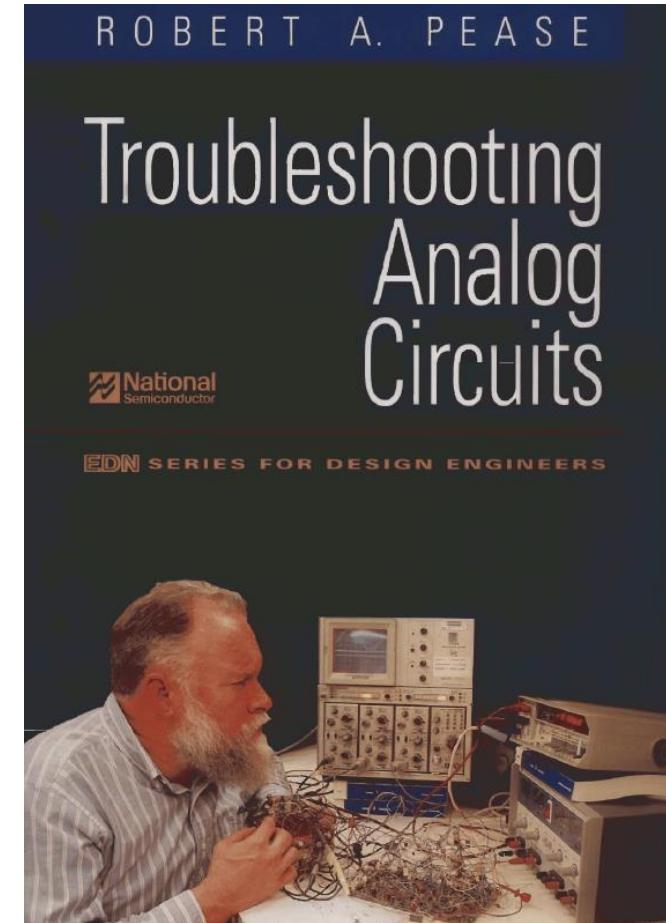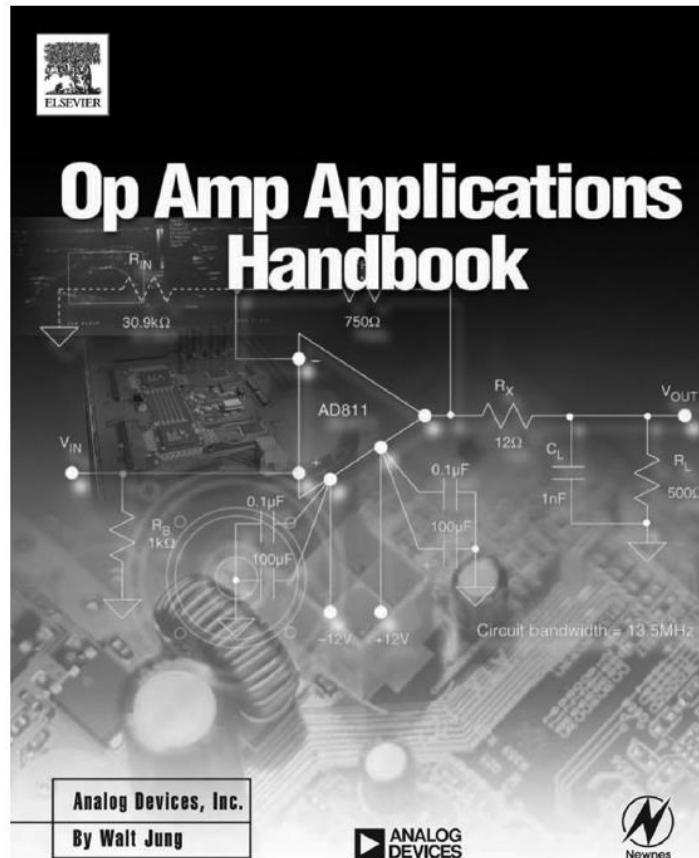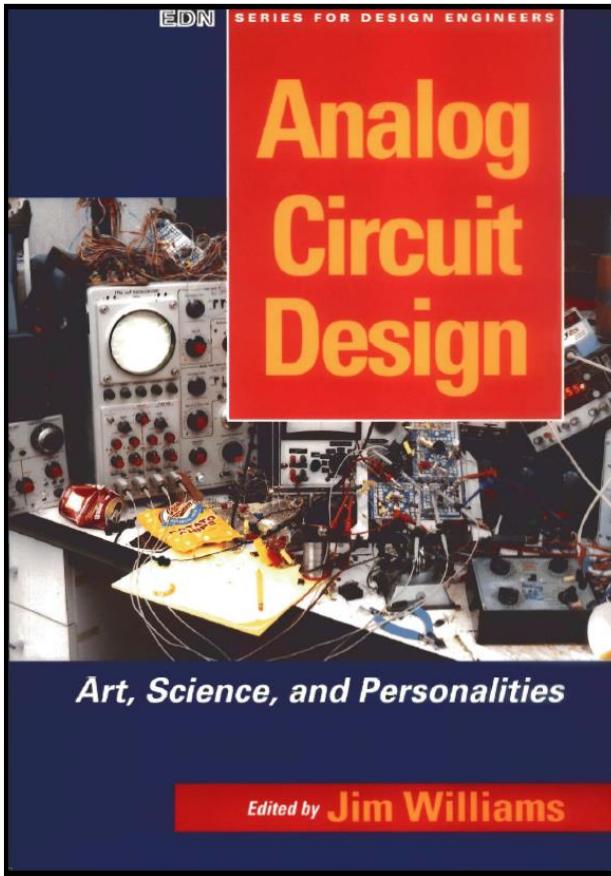The best reading: the application notes of the circuits.  
Some are written by the leading industry experts



# electronic design LIBRARY

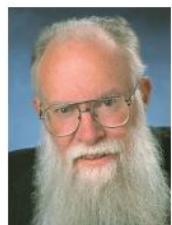

FOCUS ON:  
**BOB PEASE**  
**ON ANALOG VOL. I**

A compendium of technical articles  
from legendary *Electronic Design*  
engineer Bob Pease

Copyright © 2015 by Penton Media, Inc. All rights reserved.

[www.electronicdesign.com/home/contact/21809514/bob-pease](http://www.electronicdesign.com/home/contact/21809514/bob-pease)

[www.analog.com/media/en/training-seminars/design-handbooks/Op-Amp-Applications/SectionH.pdf](http://www.analog.com/media/en/training-seminars/design-handbooks/Op-Amp-Applications/SectionH.pdf)



Analog design :  
combination  
of art, science  
and technology.

The root is the  
operational  
amplifier.

The analog tree,  
G. Philbrick vision

